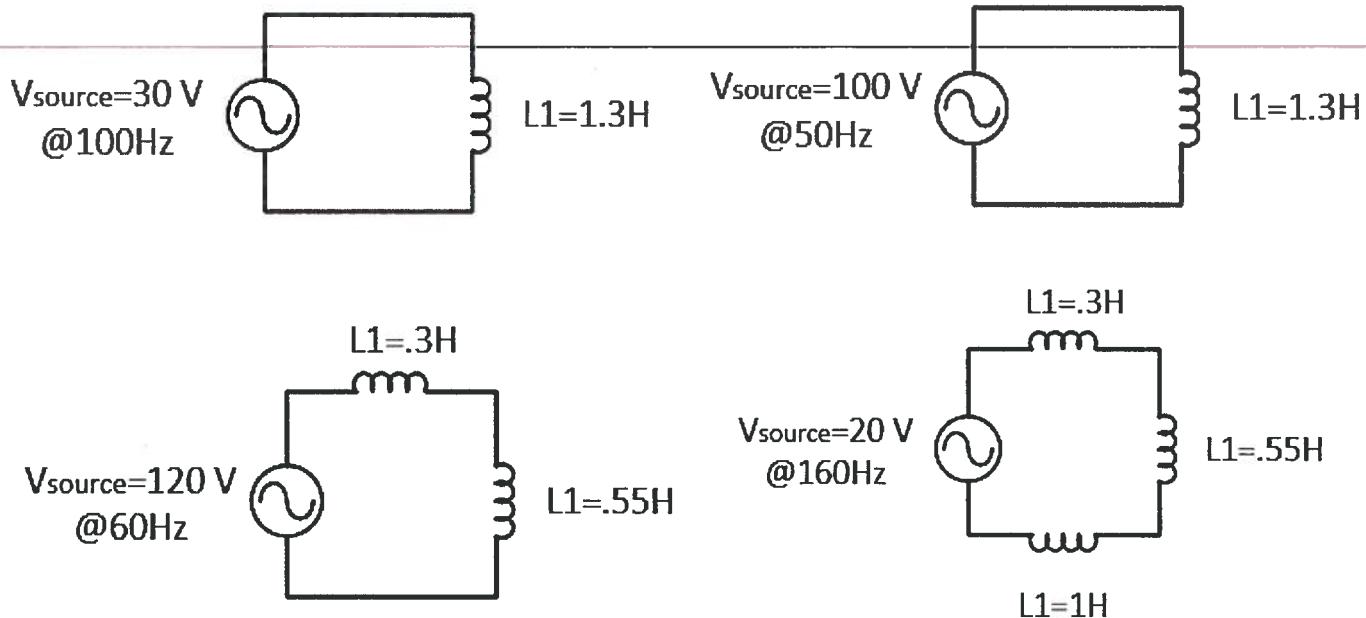


Homework B, A, C

HW - AC II Theory 10/19/18 Rasmussen Name _____

1. Solve for total current in the following circuits and for the voltages across each inductor:



2. Solve for total current in the following circuits and for the voltages across each inductor and resistor :

