

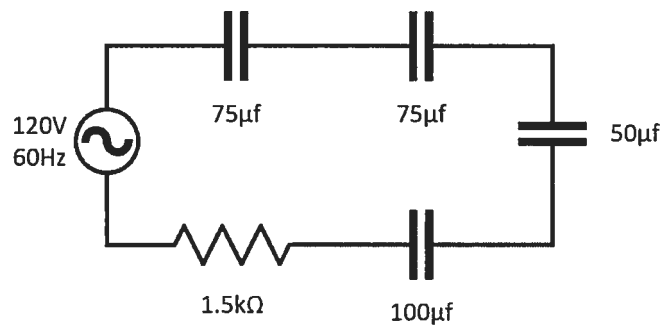
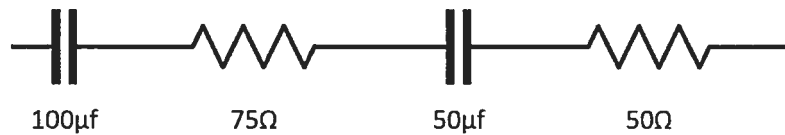


Review Chapter 6 in the book


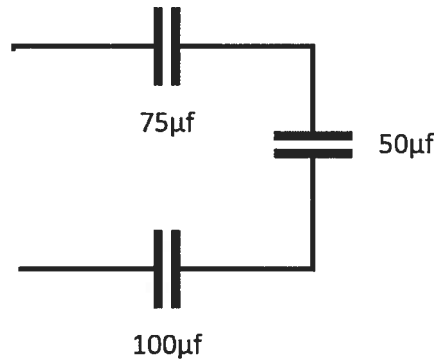
1. What is the total capacitance for the following circuits? *Write out the formula and solve*



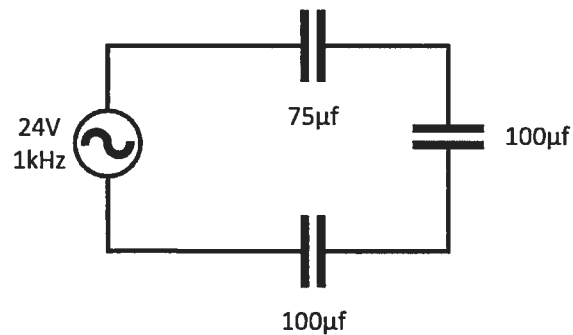2. What is the total opposition to current in this circuit? *Write out the formula and solve*




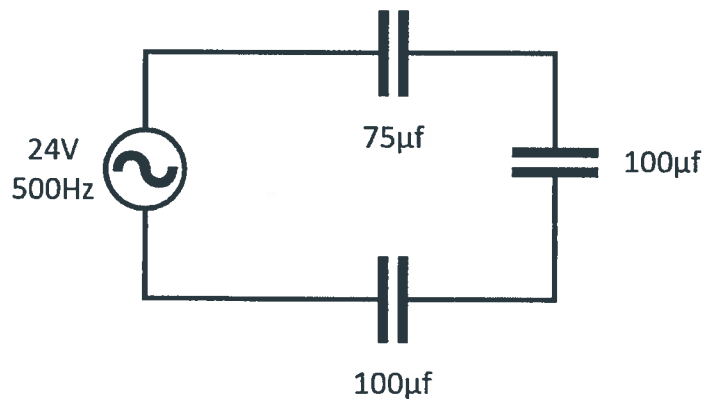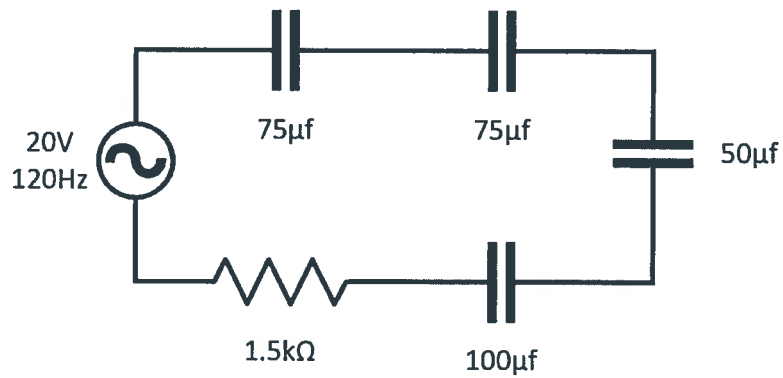3. Solve for Capacitance reactance for the following circuits. Write out the formula and solve




4. A circuit has one 100μf capacitors and two resistors, one 1.5kΩ and one 1kΩ. What is the total opposition to current (amps) in ohms in a 50V 200Hz circuit? Write out the formula and solve

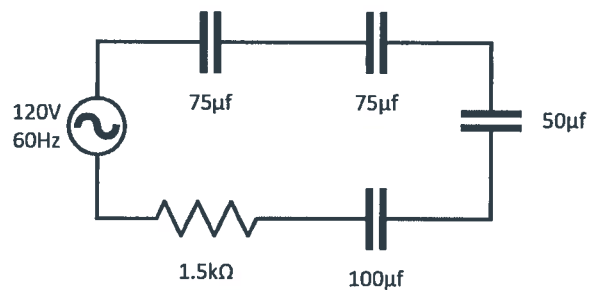5. Solve for Z for the following circuit. Write out the formula and solve




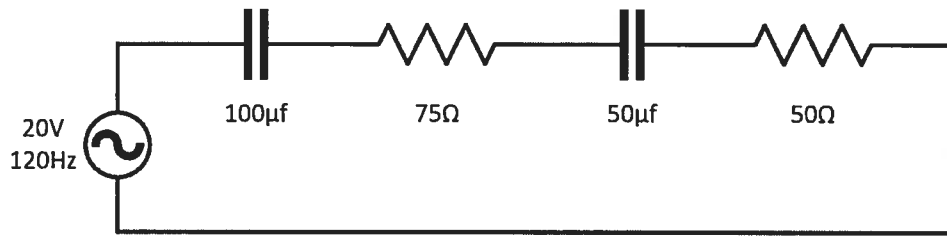6. What is the current that is flowing through the 75Ω resistor? Write out the formulas and solve



7. In the circuit above, what is the measured voltage across the 50Ω resistor? Write out the formulas and solve

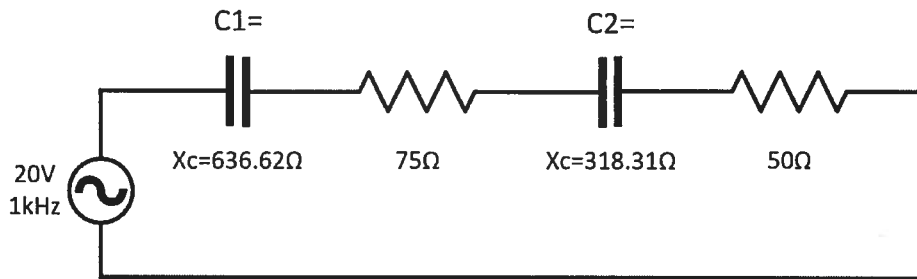
8. What are the values for C1 and C2? Write out the formulas and solve



9. In the circuit above, what is the value of the current flowing across the 50Ω resistor? Write out the formulas and solve

10. In the circuit above, what is the value of the voltage measured across C1 and C2? Write out the formulas and solve

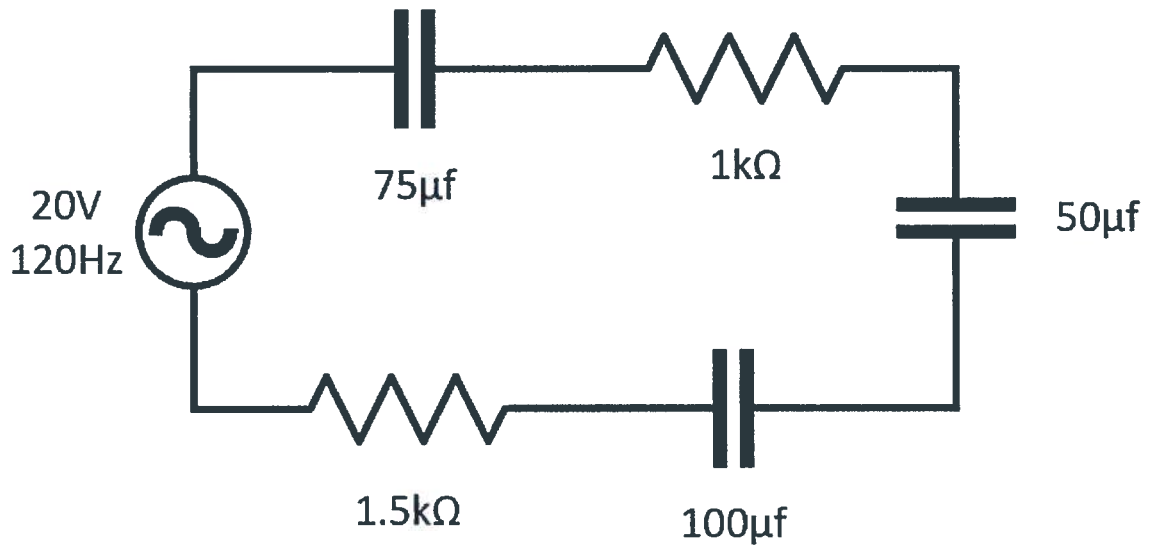11. In the circuit below, solve for the values in table. Write out the formulas and solve



Component	Voltage	Current
75µf		
1kΩ		
50µf		
100µf		
1.5kΩ		
Power Factor for this circuit		