2nd Year Circuitry Module 2 Homework

Name: _____ Job # M2 HW

Class: _____ Date: _____

Complete wiring diagram in a neat manner (no diagonal lines).

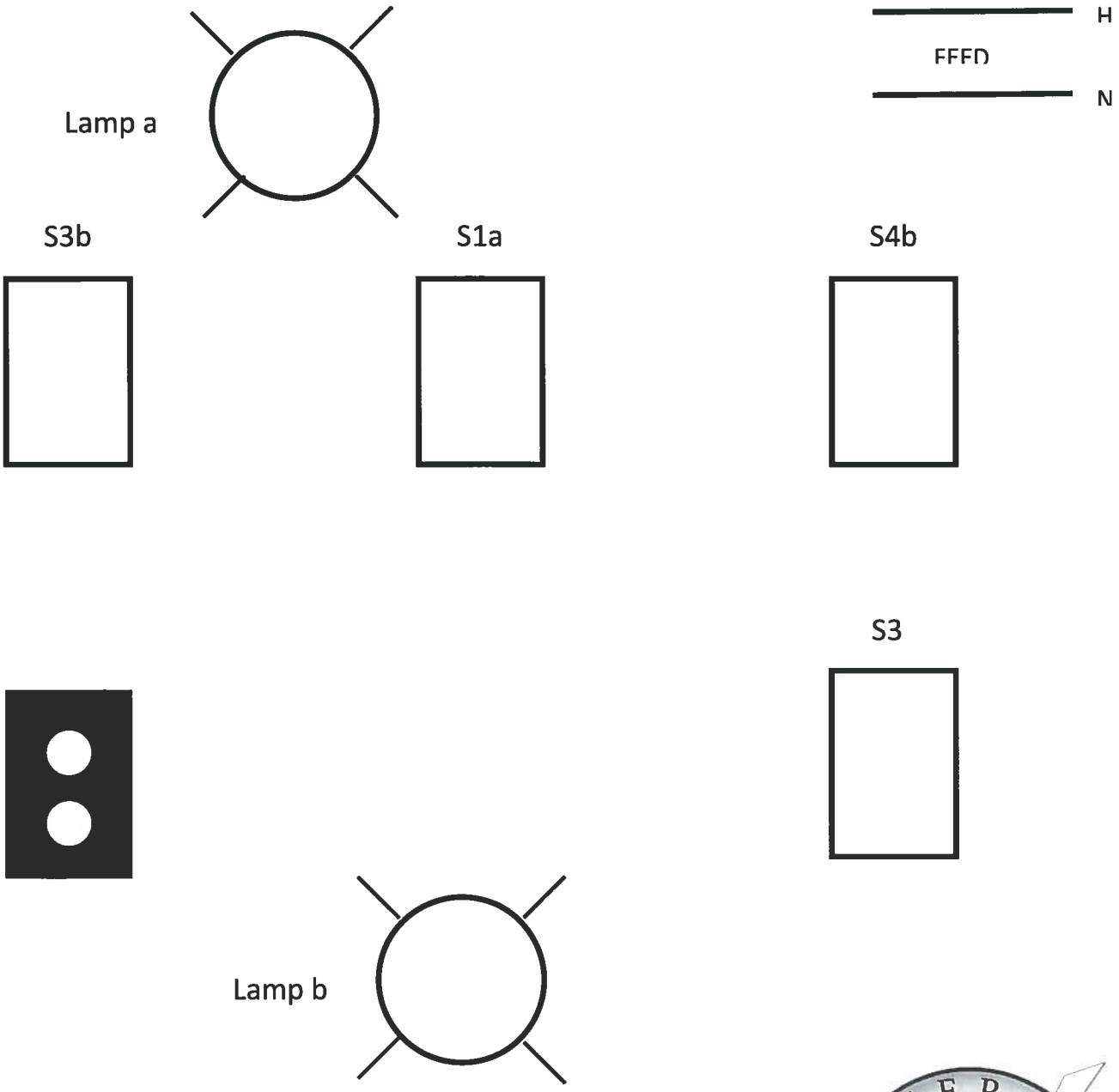

Lamp "a" controlled by S1a

Lamp "b" controlled by (2) 3-ways and (1) 4-way switches

Receptacle to be constant

Student Name: _____ Class Date: _____

Trade/Year/Section: _____ Assignment: _____

Instructor Name: _____ Materials Allowed: _____

Notes: _____